



LAB 07


**Analog IC Design – Xschem and
Master Micro Tools
gm/ID Design Methodology**

Table of Contents


Part 1: gm/ID Design Charts	3
1. NMOS Charts	3
2. PMOS Charts	4
Part 2: OTA Design	5
1. Desired Specs	5
2. OTA schematic	5
3. OTA design steps	6
4. OTA Devices Sizing	11
Part 3: Open-loop OTA simulation	11
1. OP simulation	11
Comments on OP:	12
2. Diff small signal ccs	13
3. CM small signal ccs	14
calculation of DC CM gain with hand analysis:	14
4. CMRR	15
calculation of CMRR with hand analysis:	15
5. Diff large signal ccs	16
Comments on Diff large signal:	16
6. CM large signal ccs (GBW vs VICM)	17
calculation of CM input range (CMIR) with hand analysis:	17
Part 4: Closed-Loop OTA Simulation	18
1. OP simulation	18
Comments on OP simulation:	19
2. Loop Gain	19
Comments on Compare Between Loop Gain and Open Loop:	20
3. Specs Achieved	21

Part 1: gm/ID Design Charts

1. NMOS Charts

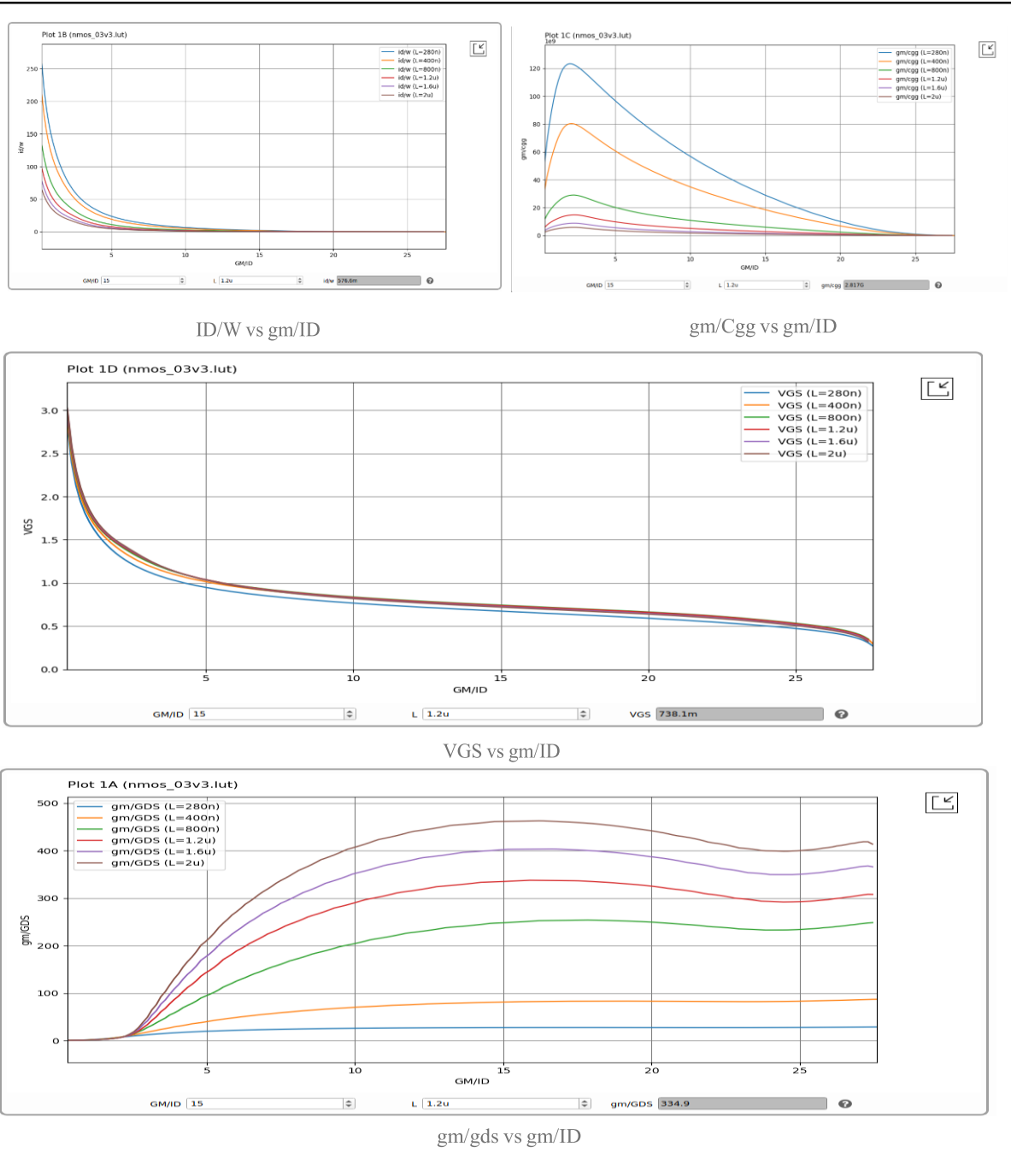

2. PMOS Charts

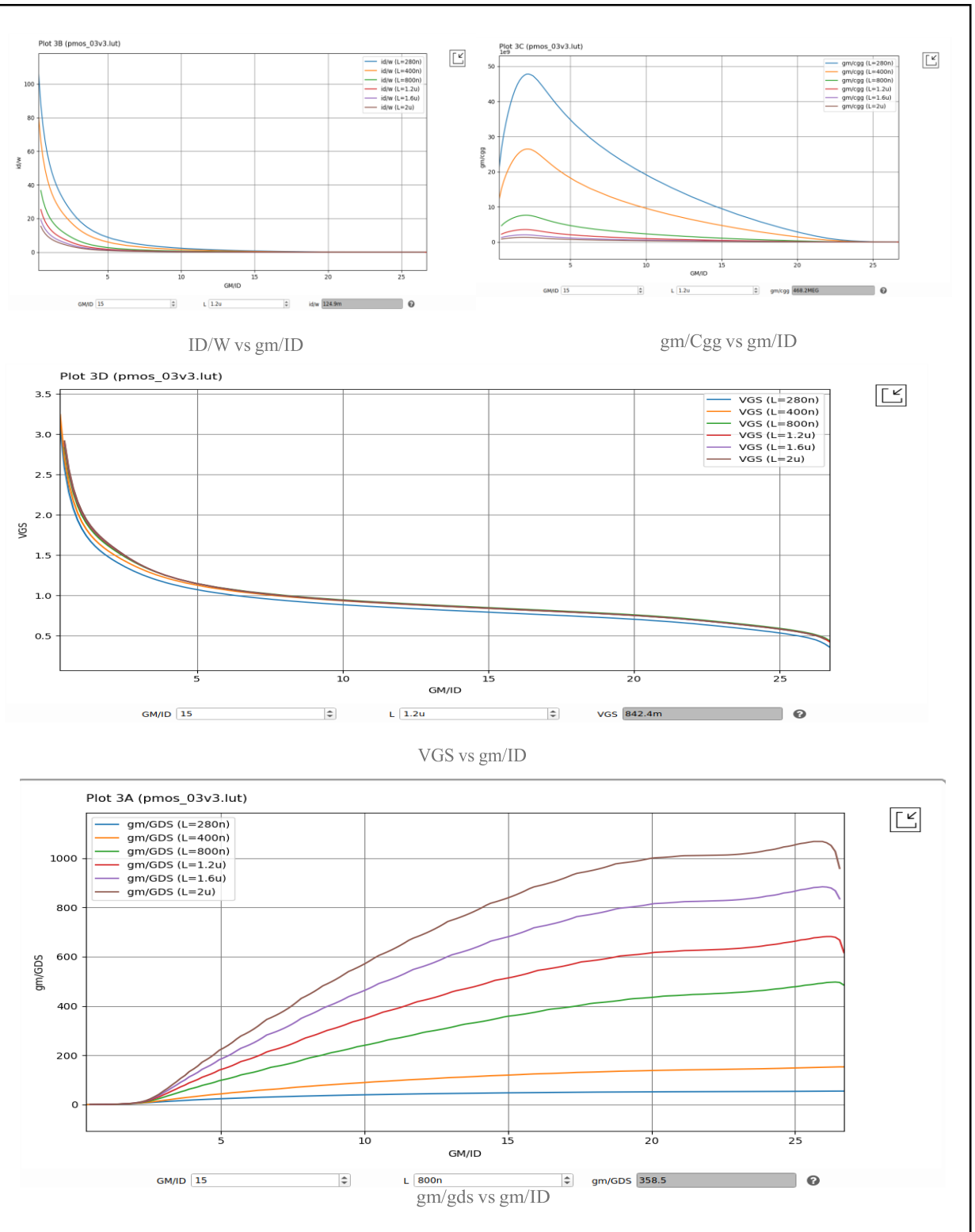

Part 2: OTA Design

1. Desired Specs

Technology	0.18 μm cmos
Supply voltage	1.8 V
Load	5 pF
Open loop dc voltage gain	≥ 34 dB
Cmrr @ dc	≥ 74 dB
Phase margin	$\geq 70^\circ$
Cm input range – low	≤ 1 V
Cm input range – high	≥ 1.5 V
GBW	≥ 10 MHz


Desired Specs

The required **gain** is **not high** (only 34 dB ≈ 50) so it can be achieved by a simple **single stage** OTA.

Since the required CMIR is close to the **supply voltage**, we need to use an **NMOS** input stage.

Since the type of input pair is **NMOS** we are going to use **sourcing** IDC connection.

2. OTA schematic

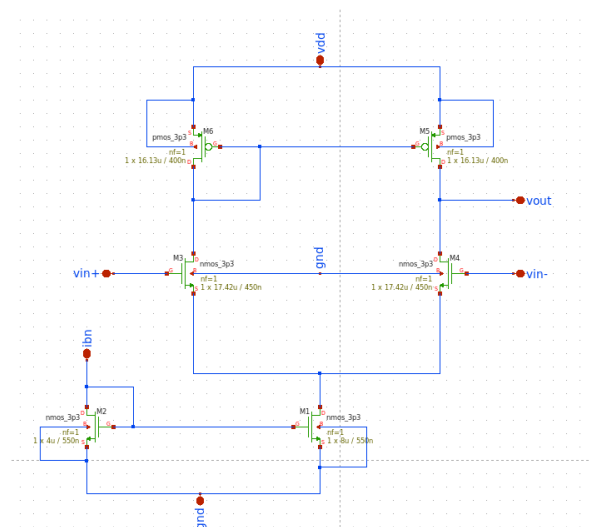

3. OTA design steps


To design 5T OTA, we can divide it into 3 stages (input, current mirror, and tail source stage).

- Design of input pair:

$$GBW = gm / 2\pi CL \Rightarrow gm = GBW * 2\pi * CL = 314.1$$


$$\text{us} \quad @ ID = 40/2 = 20 \mu A \Rightarrow gm/id = 16 S/A$$
 
$$\text{Then } Ao = gmro/2 > 50 @ gm gds > 100$$



From graph we noticed that the least L to achieve our specs is $L \approx 450$ nm

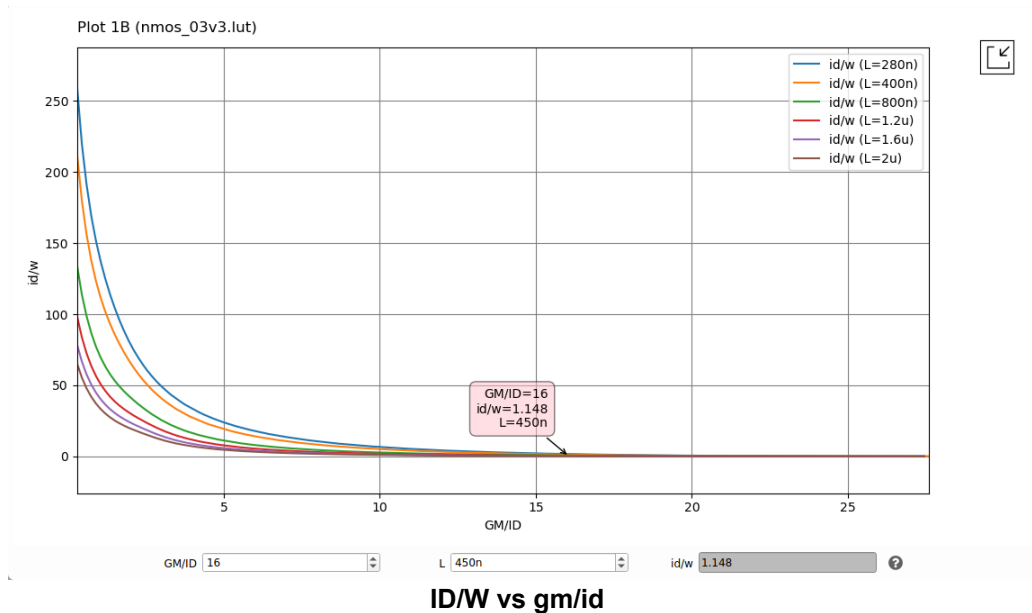
- Now we need to calculate the width of input pair
- So, we are searching for which id/w give us $gm/id = 16$, $L = 450$ nm
- from graph we noticed that $id/w = 1.148$



For $L = 450\text{nm} \Rightarrow ID/W = 1.148$ @ $ID = 20\mu\text{A}$ Then $W \approx 17.42\text{ }\mu\text{m}$

• Design of CM load:

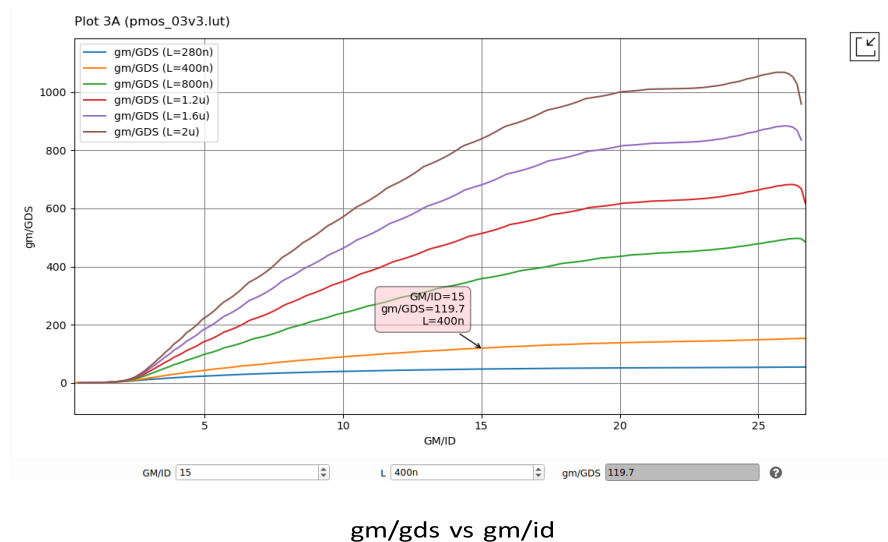By assuming equal gds of input pair = CM Load Gds5,6 < 3.14uS Let gm/id = 15 Gm = id * gm/id = 300us @ gm/gds > 95.5




$L \approx 400\text{ nm}$

Now We need to Calculate the accurate gm/id , so first we need to calculate v_{gs} For the CM Load

$$V_{incm_{Max}} < VDD - V_{GS6} + V_{TH3} \text{ Then } V_{GS6} < 1.0769 \text{ V, } V_{GS6} = 1 \text{ V}$$

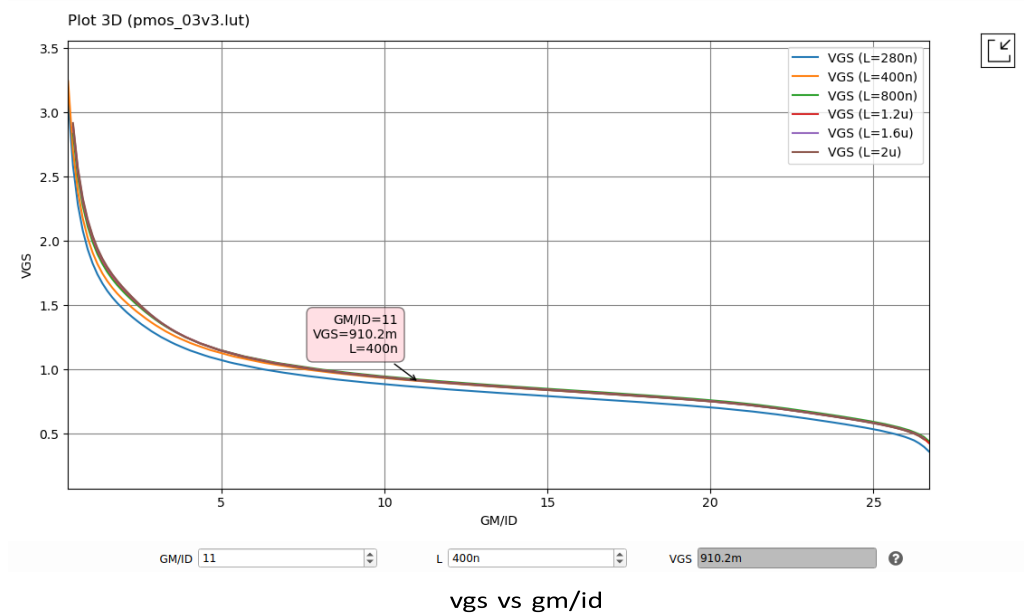
Let's see at which gm/id and $L = 0.4 \mu m$ V_{gs} will give us this value



$$gm/id = 11$$

Now we need to calculate the $width$ of CM Load so, we see which id/w give us

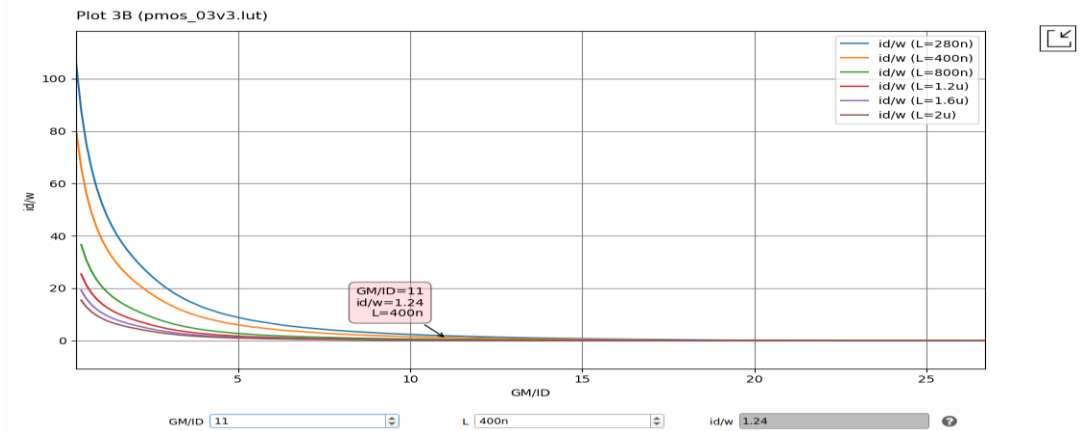$gm/id = 11$, from graph we noticed that $id/w = 1.24$ so $W = 16.13 \mu m$




ID/W vs gm/id

V_{gs} vs gm/ID

• Design of CM tail:


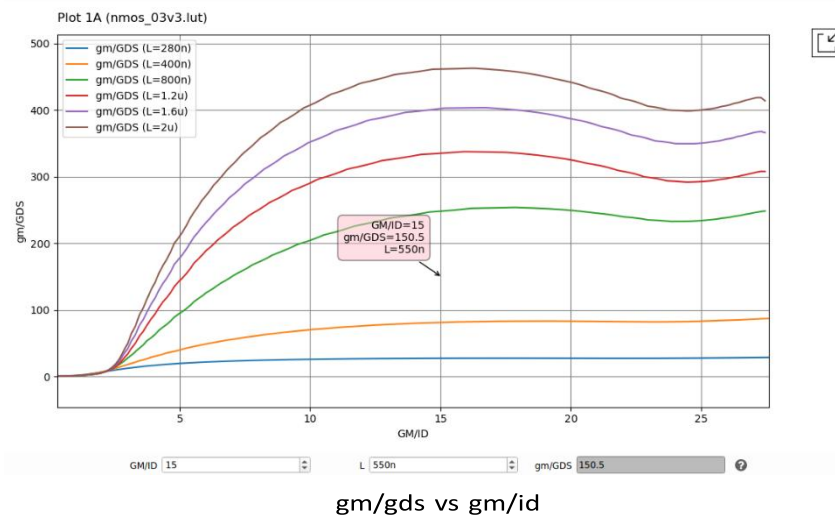
1. $A_{vd} = 50$ from the given.
2. $A_{vcm} = 9.96 \times 10^{-3} = 1/2 \cdot R_{ss} \cdot g_{m5,6} = 1/(2 \cdot R_{ss} \cdot (220 \times 10^{-6}))$.
3. the value of $R_{ss} = 228185.4691 = 1/g_{ds}$ Then $g_{ds} < 4.38 \times 10^{-6} \text{ S}$
4. Let's assume $g_{m/id} = 15$ Then $g_{m/gds} > 136.9$



gm/gds vs gm/id

L = 0.55 μm

  By applying KVL: $1 > V_{gs3,4} + v_{dsat} \rightarrow v_{dsat} < 0.2708$



$$W = 8 \text{ } \mu\text{m}$$

Now We Have Finished our specs for each part, let's do summary chart for specs.


4. OTA Devices Sizing

Param	M3,4(Input pair)	M1(CM TAIL)	M5,6(CM LOAD)
W	17.42 μm	8 μm	16.13 μm
L	0.45 μm	0.55 μm	0.4 μm
g_m	320 μs	360 μs	220 μs
I_d	20 μA	40 μA	20 μA
g_m/I_D	16	9	11
V_{GS}	729 mV	870.7 mV	911.9 mV
V_{Dsat}	99.85 mV	190.6 mV	161.2 mV
V_{ov}	25.3 mV	164.2 mV	135 mV
V^*	126.4 mV	223.8 mV	184.5 mV

OTA Devices Sizing


Part 3: Open-loop OTA simulation

1. OP simulation

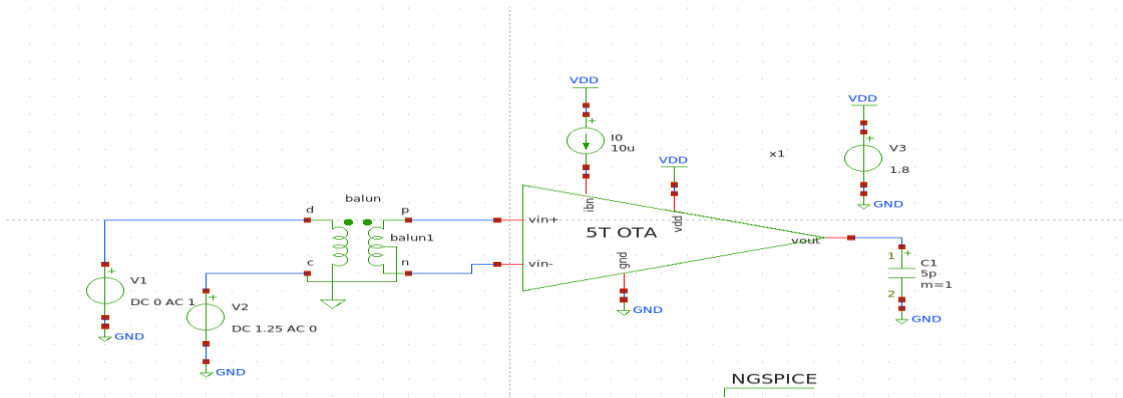

Open-loop testbench

2) DC OP For Each Transistor

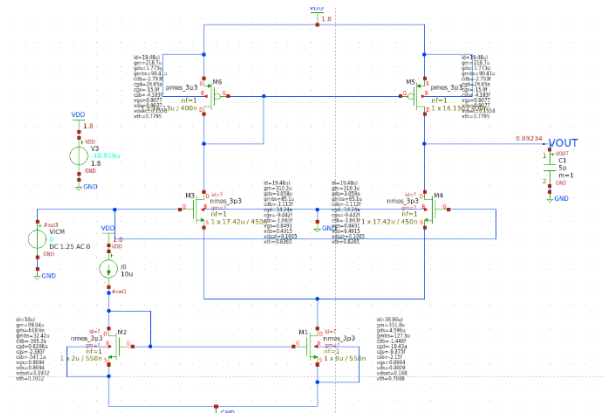

Schematic

BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm6.m0	m.x1.xm5.m0	m.x1.xm4.m0
model	pmos_3p3.12	pmos_3p3.12	nmos_3p3.12
id	1.94943e-05	1.94943e-05	1.94946e-05
gm	0.00021884	0.00021884	0.000321042
gmbs	9.04565e-05	9.04565e-05	8.77743e-05
gds	1.7743e-06	1.7743e-06	3.15388e-06
vgs	0.907724	0.907724	0.84251
vth	0.779516	0.779516	0.828319
vds	0.907723	0.907723	0.484783
vdsat	0.155492	0.155492	0.0961079

BSIM4v5: Berkeley Short Channel IGFET Model-4			
device	m.x1.xm3.m0	m.x1.xm1.m0	m.x1.xm2.m0
model	nmos_3p3.12	nmos_3p3.9	nmos_3p3.9
id	1.94946e-05	3.89887e-05	1e-05
gm	0.000321042	0.000352132	8.90372e-05
gmbs	8.77743e-05	0.000127629	3.24216e-05
gds	3.15388e-06	4.48154e-06	6.18586e-07
vgs	0.84251	0.86944	0.86944
vth	0.828319	0.708842	0.701212
vds	0.484783	0.407477	0.869433
vdsat	0.0961079	0.188044	0.193168

DC OP parameters

vout = 8.923424e-01


Vout

Comments on OP:

Comment:

- The current and gm in the input pair are exactly equal.
- $V_{out} = V_{DD} - V_{DS5} = V_{DD} - V_{GS6} = 0.892 \text{ V}$ because the current in both Transistors are equal because no mismatch.

2. Diff small signal ccs

 

diff gain bode plot (magnitude)

```
gain = 6.487973e+01 at= 1.000000e+00
bw = 1.548170e+05
gbw = 1.004449e+07
```


diff small signal results

$$diff\ gain = gm_{3,4}(ro_{5,6}/ro_{3,4}), BW = \frac{1}{2\pi R_{out} \cdot CL}, GBW = \frac{gm_{3,4}}{2\pi CL}$$

Spec	Simulation	Hand analysis
DC diff gain	36.24 dB	36.27 dB
BW	154.81 KHz	156.86 KHz
GBW	10.04 MHz	10.2 MHz

simulation vs hand analysis

3. CM small signal ccs

 

cmgain = 7.871319e-03 at= 1.000000e+00

CM gain Results


calculation of DC CM gain with hand analysis:

$$A_{vcm} = \frac{1}{2g_{m5,6} \cdot r_{o1}} = -40.81 \text{ dB}$$

Spec	Simulation	Hand analysis
DC CM gain	-41.87 dB	-40.81 dB

simulation vs hand analysis

4. CMRR

 



calculation of CMRR with hand analysis:

$$\text{CM Gain} = \frac{1}{2 \cdot g_{m5} \cdot r_{o1}}, \text{Diff Gain} = \frac{g_{m3} \cdot r_{o5} \cdot r_{o3}}{r_{o5} + r_{o3}}, \text{CMRR} = \frac{A_{vd}}{A_{cm}} = 7152.5$$

Spec	Simulation	Hand analysis
CMRR	78.6 dB	$A_{vd} - A_{vCM} = 77.09 \text{ dB}$

simulation vs hand analysis

5. Diff large signal ccs

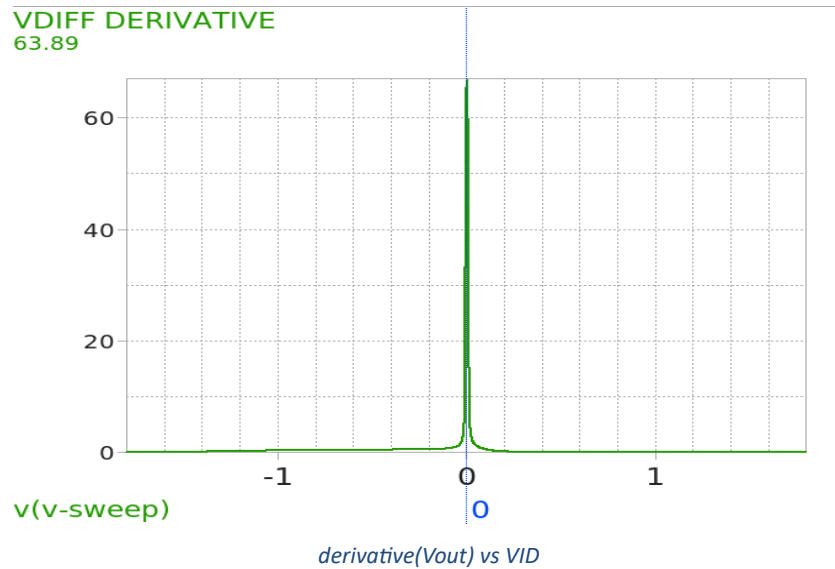 


Comments on Diff large signal:

Comment:

- The value of V_{out} @ ($V_{ID} = 0$) = 0.8923, Because at $V_{ID} = 0$, the currents in both branches are equal, since there is no mismatch or differential input and all four transistors operate in saturation with approximately equal r_o values. As a result, a voltage divider is formed through these equal resistances, producing a supply voltage equal to VDD.
- simulation $A_{vd} = 64.87$, peak = 63.89 they are the same.

6. CM large signal ccs (GBW vs VICM)

 

vcm_min = 9.200000e-01
vcm_max = 1.720000e+00

CMIR

calculation of CM input range (CMIR)with hand analysis:

$$V_{GS3,4} + V_{DSsat1} < VICMR < VDD - V_{GS5,6} - V_{DSsat3,4} + V_{GS3,4}$$


$$1 < VICMR < 1.64$$

Spec	Analytical	Simulation
Vcm max	1.64	1.72
Vcm min	1	0.92


Part 4: Closed-Loop OTA Simulation

1. OP simulation

1) Schematic of the OTA

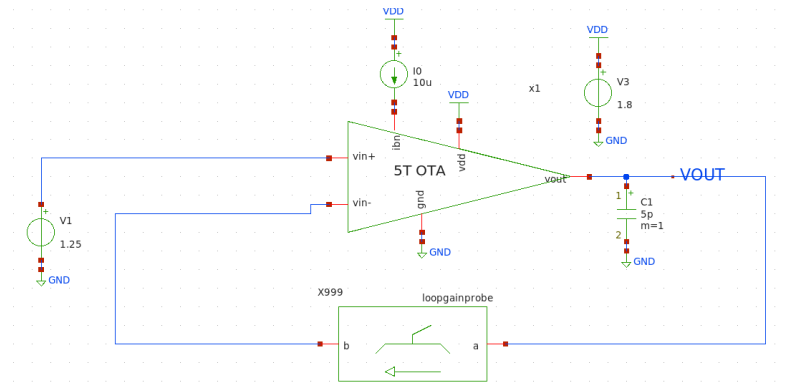

2) DC OP For Each Transistor

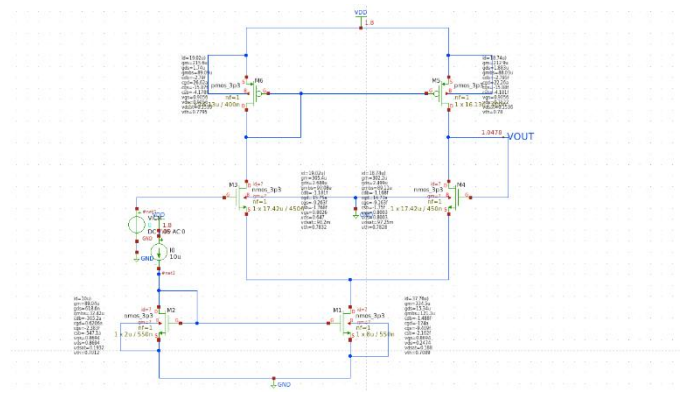

Schematic

BSIM4v5: Berkeley Short Channel IGFET Model-4					
device	m.x1.xm6.m0	m.x1.xm5.m0	m.x1.xm4.m0		
model	pmos_3p3.12	pmos_3p3.12	nmos_3p3.12		
id	1.82861e-05	1.81641e-05	1.81641e-05		
gm	0.000210397	0.000209201	0.00030474		
gmbs	8.69514e-05	8.64814e-05	9.23255e-05		
gds	1.68567e-06	1.74376e-06	2.53333e-06		
vgs	0.902139	0.902139	0.774434		
vth	0.779532	0.779734	0.767329		
vds	0.902138	0.830995	0.774433		
vdsat	0.151361	0.151213	0.0918029		
BSIM4v5: Berkeley Short Channel IGFET Model-4					
device	m.x1.xm3.m0	m.x1.xm1.m0	m.x1.xm2.m0		
model	nmos_3p3.12	nmos_3p3.9	nmos_3p3.9		
id	1.82861e-05	3.64502e-05	1e-05		
gm	0.000306293	0.000309144	8.90372e-05		
gmbs	9.28024e-05	0.000112406	3.24216e-05		
gds	2.61338e-06	3.89723e-05	6.18586e-07		
vgs	0.775432	0.86944	0.86944		
vth	0.767504	0.708974	0.701212		
vds	0.70329	0.194555	0.869433		
vdsat	0.0922059	0.187947	0.193168		


DC OP parameters

Comments on OP simulation:


Comment:

- the current and gm in the input pair is not exactly equal, that's because Negative feedback circuits inherently exhibit static gain error, which leads to mismatch in the input pair.
- $\Delta gm1 = 306.29\mu - 304.74\mu = 1.55\mu S$, Mismatch = 0.5%
- $\Delta I_{D1} = 18.28\mu - 18.16\mu = 0.12\mu A$, Mismatch = 0.65%

2. Loop Gain

 

loop gain bode plot (magnitude)

 

loop gain bode plot (phase)

```
gain          = 6.461535e+01 at= 1.000000e+02
bw            = 1.538918e+05
gbw = 9.943773e+06
gain_crossover_freq = 9.937795e+06
phaseatzerogain  = 9.001850e+01
pm = 8.998150e+01
```

• Compare Between Loop Gain and Open Loop:

	OPEN LOOP	LOOP GAIN
A_v	36.24dB	36.24dB
GBW	10M	9.94M

Comments on Compare Between Loop Gain and Open Loop:

Comment:

- Gain is **Equal** because **Beta** is approximately Equal to 1. But **GBW** in Loop Gain is **lower** due to:
 - Parasitic capacitances and resistances** in the circuit introduce additional poles and zeros, which reduce the high-frequency response and lower the measured **GBW** in loop gain.
 - $GBW_{loop} \approx \beta \cdot GBW_{open-loop}$, since the feedback factor β is not exactly ideal and slightly less than 1, the loop gain is proportionally reduced, leading to a slightly lower **GBW** compared to the open-loop case.

• Hand analysis results

$$A_{vd} = gm(ro5 \parallel ro3) = 65.1 = 36.27 \text{ dB}, BW = \frac{1}{2\pi R_{out} \cdot C_L} = 156.86 \text{ KHz}$$

$$GBW = A_{vd} \cdot BW = 10.02 \text{ MHz}, A_{oL} = 65.1, LG = \beta A_{oL}, \beta = 1 \therefore LG = 65.1 = 36.27 \text{ dB}$$

$$A_{cl} = \frac{A_{oL}}{1 + \beta A_{oL}} = 0.984, PM = 90^\circ, \text{ because we have one dominant pole.}$$

	Simulation	Hand Analysis
A_{oL}	36.24dB	36.27dB
BW	153.8k	156.86k
GBW	10M	10.02M
LG	36.24dB	36.27dB
PM	90°	90°
A_{vcl}	0.984	0.984

3. Specs Achieved

Technology	Specs	Achieved
open loop DC Voltage gain	$\geq 34\text{dB}$	36.24 dB
CMRR	$\geq 74\text{dB}$	$\approx 78.32\text{dB}$
Phase margin	$\geq 70^\circ$	90°
CM input range-low	$\leq 1\text{V}$	0.92 V
CM input range-high	$\geq 1.5\text{V}$	1.72 V
GBW	$\geq 10\text{MHz}$	10.04 MHz